

Brian Gaur DCD HW #3 Section #4 RUID: 150003563

#1) Implement the following circuits in a hazard-free manner

a.)  $F(A,B,C) = B\bar{C} + \bar{A}C$

C \ AB	00 01 11 10			
	0	1	1	0
0	0	1	1	0
1	1	1	0	0

This is the prime implicant to include to eliminate timing hazards

New Minimal Sum  $\rightarrow B\bar{C} + \bar{A}C + \bar{A}B$

b.)  $F(A,B,C,D) = \Sigma(0,4,5,6,7,9,11,13,14)$

CD \ AB	00 01 11 10			
	0	1	1	0
00	1	1	0	0
01	0	1	1	1
11	0	1	0	1
10	0	1	1	0

$F = \bar{A}\bar{C}\bar{D} + \bar{A}B + B\bar{C}\bar{D} + A\bar{C}D + B\bar{C}D + A\bar{B}D$

#2) Draw K-map, # of Prime Implicants, Distinguished One-Cells, essential primes, find minimal sum.

a.)  $F = \Sigma_{WXYZ}(0,1,5,7,8,9,13)$

- 3 Prime Implicants

- 4 Distinguished One-Cells

- 3 Essential Primes

$F = X'Y' + Y'Z + WXZ$

YZ \ WX	00 01 11 10			
	0	1	1	0
00	*1	0	0	1*
01	1	1	*1	1
11	0	1*	0	0
10	0	0	0	0

b.)  $F = \Sigma_{WXYZ}(0,1,2,3,6,7,8,13,14,15)$

- 5 Prime Implicants

- 4 Distinguished One-Cells

- 4 Essential Prime Implicants

$F = \bar{W}\bar{X} + XY + WXZ + \bar{X}\bar{Y}\bar{Z}$

YZ \ WX	00 01 11 10			
	0	1	1	0
00	1	0	0	1*
01	*1	0	1*	0
11	1	1	1	0
10	1	1	*1	0



c.)  $F = \sum_{w,x,y,z} (0, 2, 3, 4, 5, 6, 7, 10, 11, 13)$

$yz \backslash wx$	00	01	11	10
00	1*	1	0	0
01	0	1	*1	0
11	1	1	0	1*
10	1	1	0	1*

- 4 Distinguished One-Cells

- 5 Prime Implicants

- 3 Essential Primes

$$F = \bar{w}x + \bar{x}\bar{y} + \bar{w}\bar{y}\bar{z} + x\bar{y}z$$

d.)  $F = \sum_{w,x,y,z} (1, 3, 5, 7, 11, 12, 13, 14, 15)$

$yz \backslash wx$	00	01	11	10
00	0	0	*1	0
01	1*	1	1	0
11	1	1	1	*1
10	0	0	*1	0

- 4 Distinguished One-Cells

- 4 Prime Implicants

- 3 Essential Primes

$$F = wx + yz + \bar{w}z$$

#3)  $F = \sum_{w,x,y,z} (3, 4, 6, 7, 8, 10, 11, 12)$

a.) Use K-map to find minimum Product of Sums

$yz \backslash wx$	00	01	11	10
00	0	1	1	1
01	0	0	0	0
11	1	1	0	1
10	0	1	0	1

Product of sums

$$= (y' + z)(w' + x' + z')(w + x + y)$$

$$= (y + z')(w + x + z)(w' + x' + y')$$

b.) (Next Page)


$$F = wx + xy + xz + \bar{w}z$$



[Pg Two]

$$(Y + Z')X(W + X' + Z)(W' + X' + Y)$$

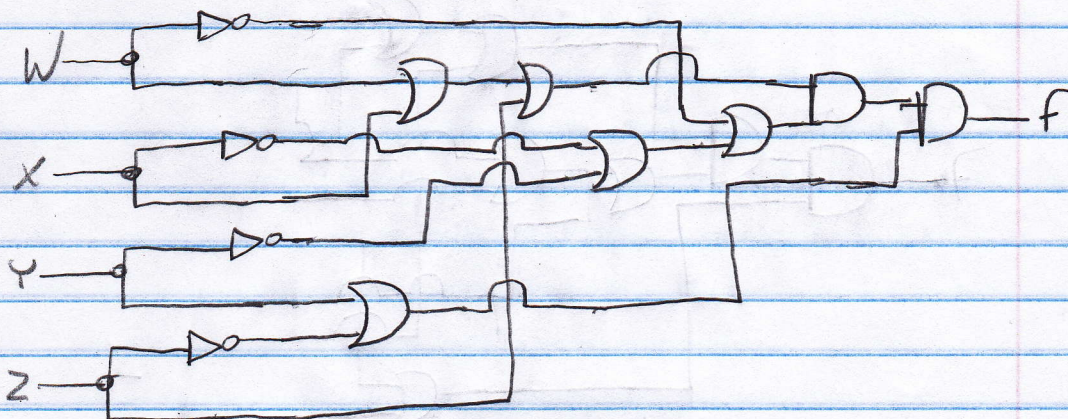b.) Draw logic diagram implementing product-of-sums



c.) Are there any static hazards? Static-1 or Static-0?

Wx \ Yz	00	01	11	10
00	1	1	1	1
01	1	0	1	0
11	1	1	1	1
10	1	1	0	1

Yes, two static-0 hazards, denoted by  $\diamond$

d.) To fix the design, need to add in two extra terms to the product-of-sums expression to cover the two hazards

→ These two expressions are found using Product of sums standard method for the diamonds I circled in the prior question

$$\text{Original } F = (Y + Z')(W + X + Z)(W' + X' + Y')$$

$$\text{W/O Hazards} = \boxed{(Y + Z')(W + X + Z)(W' + X' + Y')(W' + X' + Z')(W + X + Y) = F}$$