



ECE-332:437




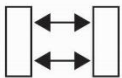
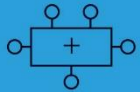

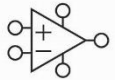
 

DIGITAL SYSTEMS DESIGN (DSD)

Fall 2016 – Lecture 4

Nagi Naganathan
September 15, 2016

Chapter 2 :: Topics

- Introduction
- Boolean Equations
- Boolean Algebra
- From Logic to Gates
- Multilevel Combinational Logic
- X's and Z's, Oh My
- Karnaugh Maps
- Combinational Building Blocks
- Timing

Application Software	
Operating Systems	
Architecture	
Micro-architecture	
Logic	
Digital Circuits	
Analog Circuits	
Devices	
Physics	

Combinatorial Building Blocks

Combinational Building Blocks


- Multiplexers
- De-Multiplexers
- Decoders
- Encoders

Selecting

- **Selecting of data or information is a critical function in digital systems and computers**
- **Circuits that perform selecting have:**
 - **A set of information inputs from which the selection is made**
 - **A single output**
 - **A set of control lines for making the selection**
- **Logic circuits that perform selecting are called *multiplexers***
- **Selecting can also be done by three-state logic or transmission gates**

Multiplexor (Mux)




 
- Mux: Another popular combinational building block
 - Routes one of its N data inputs to its one output, based on binary value of select inputs
 - 4 input mux \rightarrow needs 2 select inputs to indicate which input to route through
 - 8 input mux \rightarrow 3 select inputs
 - N inputs $\rightarrow \log_2(N)$ selects
 - Like a rail yard switch



Multiplexers


- A multiplexer selects information from an input line and directs the information to an output line
- A typical multiplexer has n control inputs (S_{n-1}, \dots, S_0) called *selection inputs*, 2^n information inputs (I_{2^n-1}, \dots, I_0), and one output Y
- A multiplexer can be designed to have m information inputs with $m < 2^n$ as well as n selection inputs

Mux Internal Design

  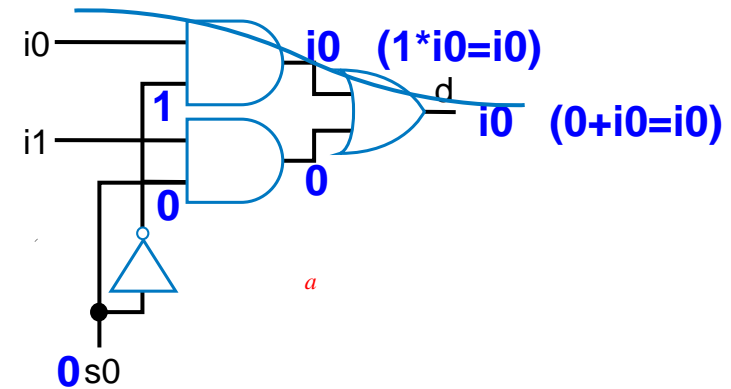 


Mux Example

 - City mayor can set four switches up or down, representing his/her vote on each of four proposals, numbered 0, 1, 2, 3
- City manager can display any such vote on large green/red LED (light) by setting two switches to represent binary 0, 1, 2, or 3
- Use 4x1 mux




Muxes Commonly Together – N-bit Mux

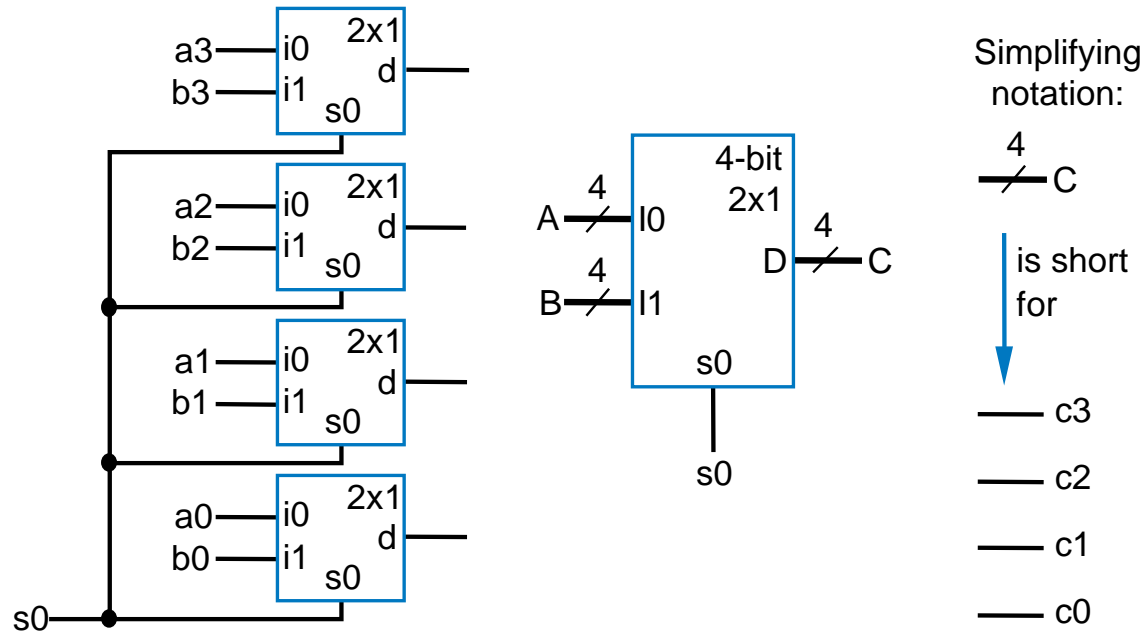

- Ex: Two 4-bit inputs, A (a3 a2 a1 a0), and B (b3 b2 b1 b0)
 - 4-bit 2x1 mux (just four 2x1 muxes sharing a select line) can select between A or B



N-bit Mux Example

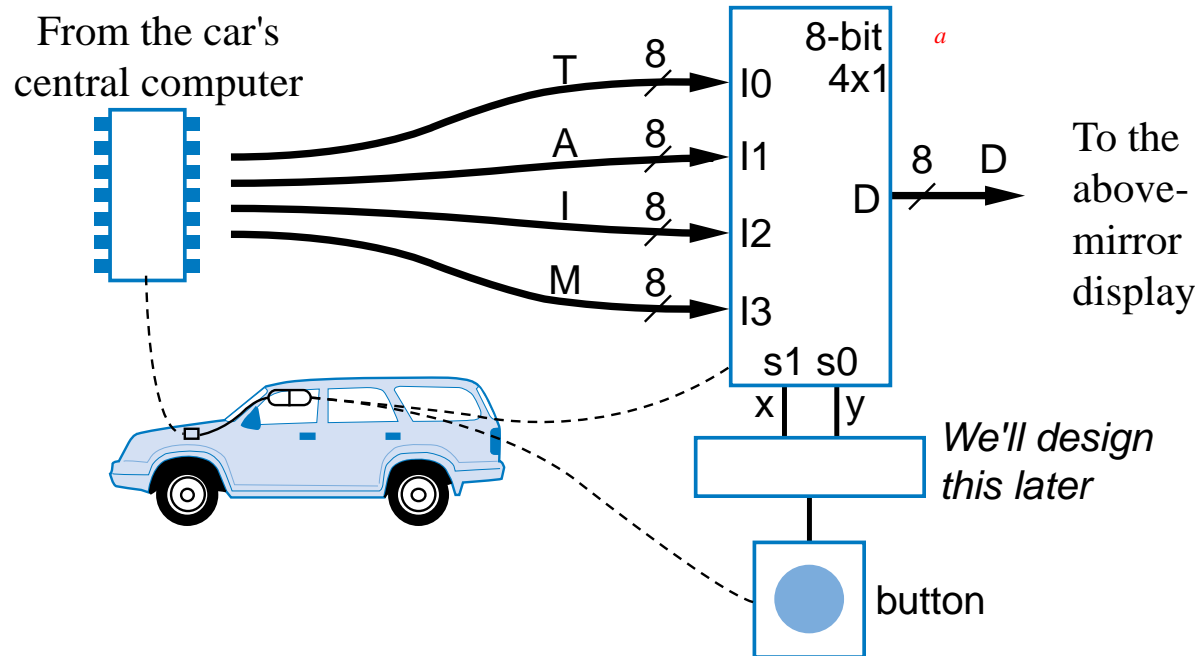


- Four possible display items
 - Temperature (T), Average miles-per-gallon (A), Instantaneous mpg (I), and Miles remaining (M) – each is 8-bits wide
 - Choose which to display on D using two inputs x and y
 - Pushing button sequences to the next item
 - Use 8-bit 4x1 mux



Multiplexer (Mux)

- Selects between one of N inputs to connect to output
- $\log_2 N$ -bit select input – control input
- Example:

2:1 Mux

 

S	D_1	D_0	Y	S	Y
0	0	0	0	0	D_0
0	0	1	1	1	D_1
0	1	0	0		
0	1	1	1		
1	0	0	0		
1	0	1	0		
1	1	0	1		
1	1	1	1		


Multiplexer Implementations

- **Logic gates**

- Sum-of-products form


Y S	$D_0 D_1$			
	00	01	11	10
0	0	0	1	1
1	0	1	1	0

$$Y = D_0 \bar{S} + D_1 S$$

 

- **Tristates**

 - For an N-input mux, use N tristates
- Turn on exactly one to select the appropriate input




Logic using Multiplexers

- Using the mux as a lookup table


<i>A</i>	<i>B</i>	<i>Y</i>
0	0	0
0	1	0
1	0	0
1	1	1

$$Y = AB$$

 

Logic using Multiplexers

- Reducing the size of the mux

 


2-to-1-Line Multiplexer

- Since $2 = 2^1$, $n = 1$
- The single selection variable S has two values:
 - $S = 0$ selects input I_0
 - $S = 1$ selects input I_1

- The equation:

$$Y = \bar{S}I_0 + SI_1$$

- The circuit:

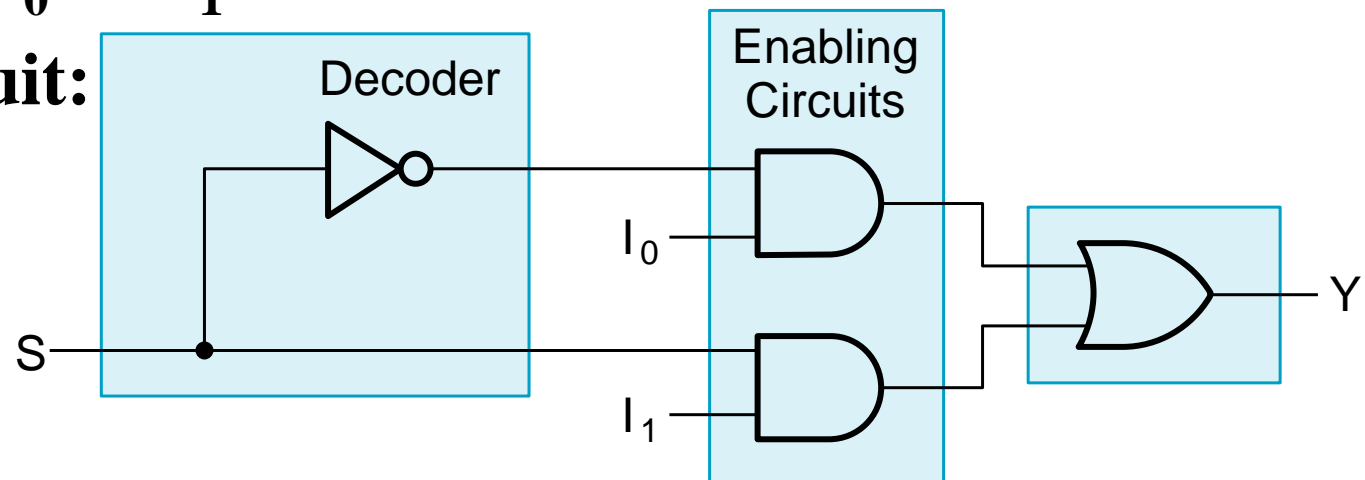


2-to-1-Line Multiplexer (continued)

- **Note the regions of the multiplexer circuit shown:**
 - 1-to-2-line Decoder
 - 2 Enabling circuits
 - 2-input OR gate
- **To obtain a basis for multiplexer expansion, we combine the Enabling circuits and OR gate into a 2×2 AND-OR circuit:**
 - 1-to-2-line decoder
 - 2×2 AND-OR
- **In general, for an 2^n -to-1-line multiplexer:**
 - n -to- 2^n -line decoder
 - $2^n \times 2$ AND-OR

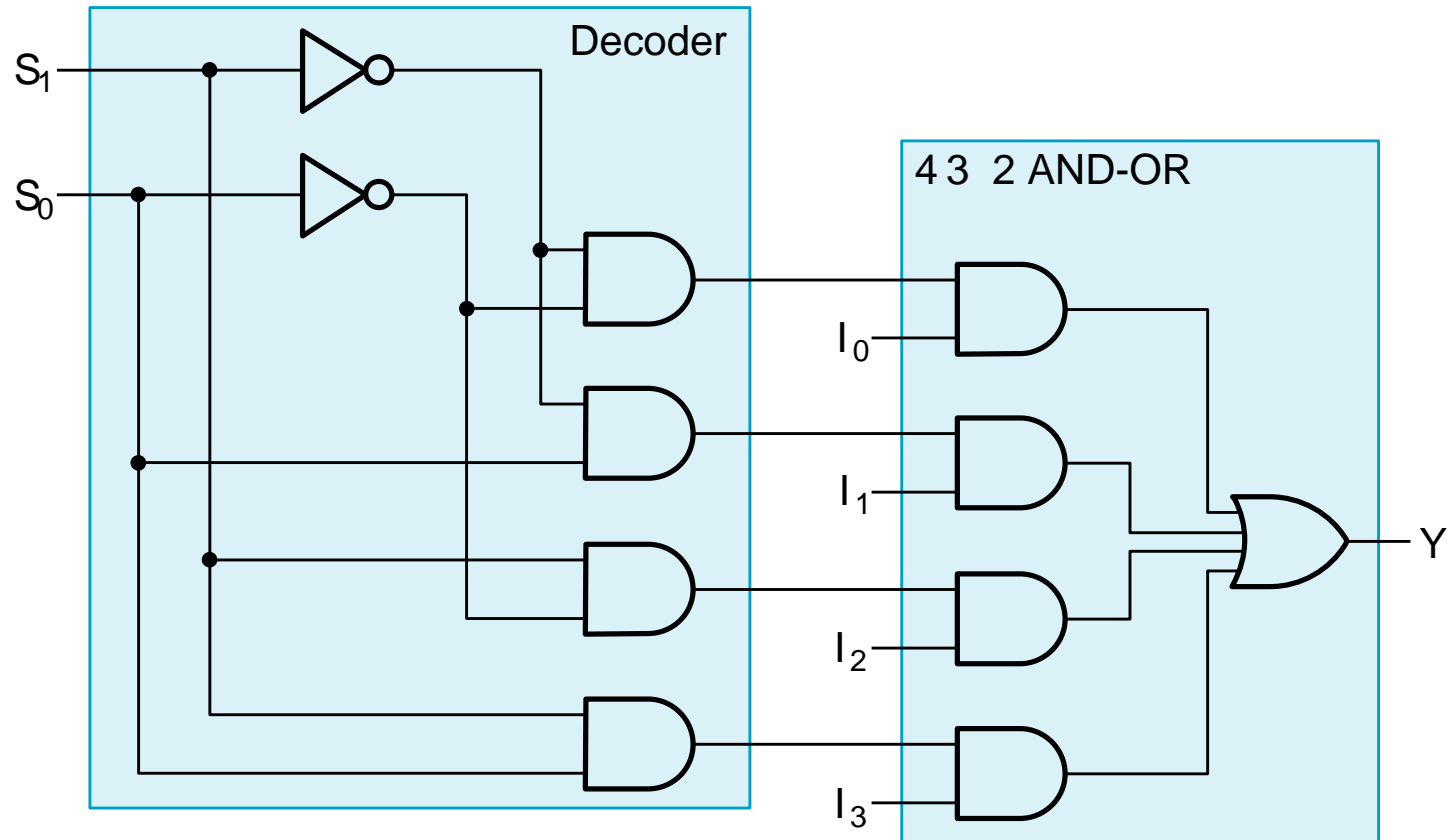
Example: 4-to-1-line Multiplexer

- 2-to- 2^2 -line decoder
- $2^2 \times 2$ AND-OR




Multiplexer Width Expansion

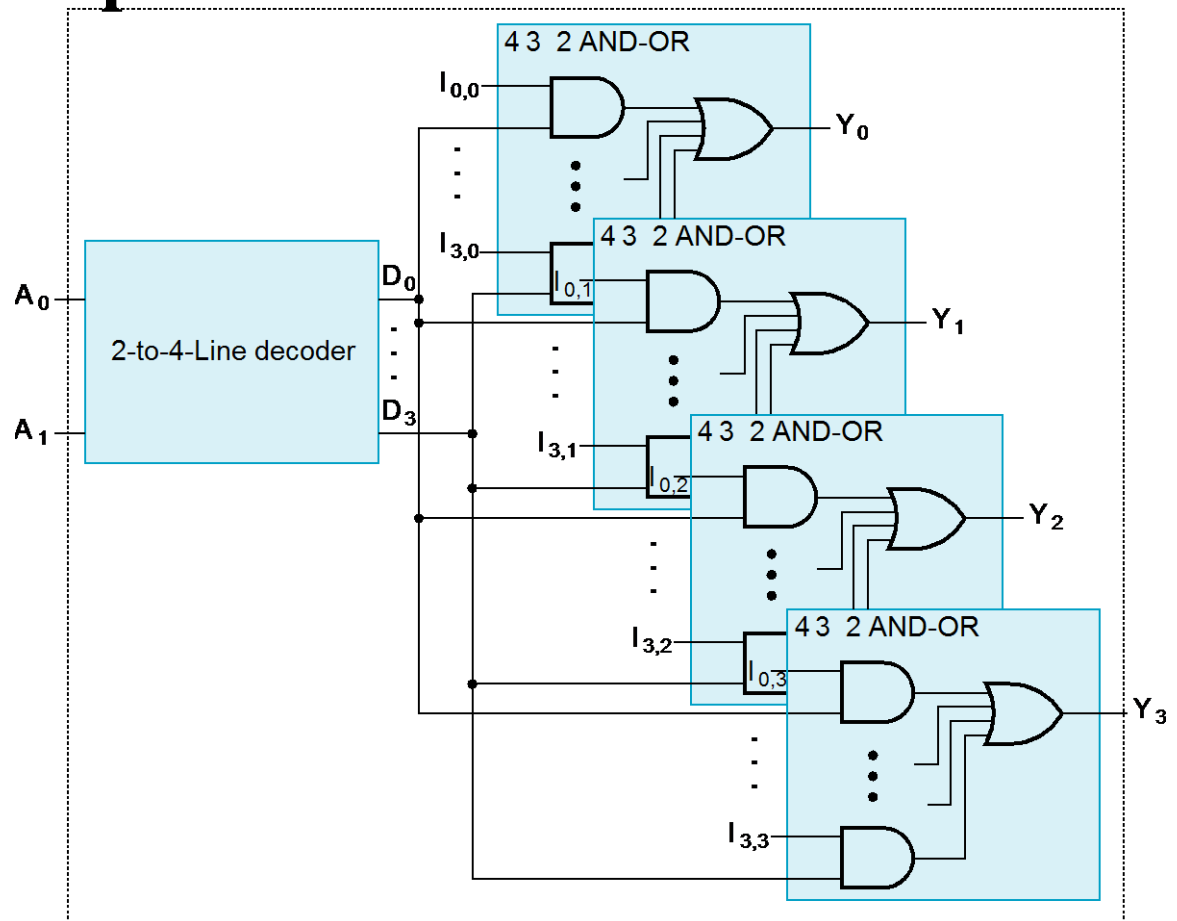- Select “vectors of bits” instead of “bits”
- Use multiple copies of $2^n \times 2$ AND-OR in parallel
- Example:
4-to-1-line quad multi-plexer



Other Selection Implementations

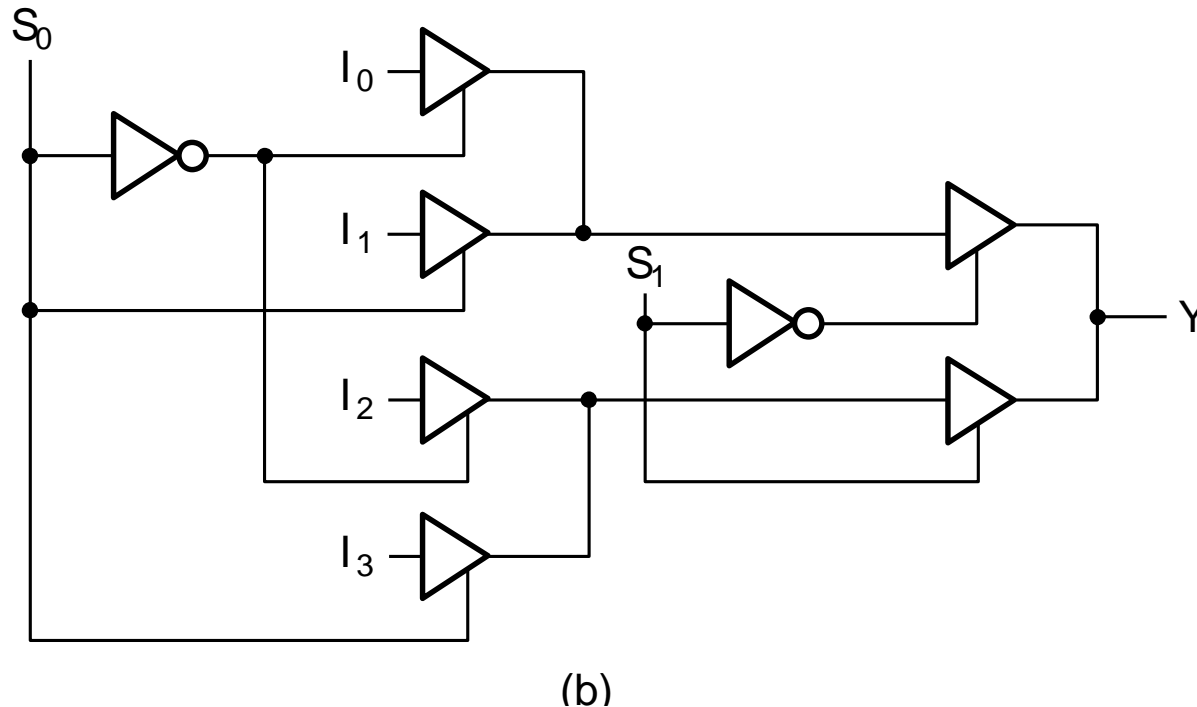- **Three-state logic in place of AND-OR**





- **Gate input cost = 14 compared to 22 (or 18) for gate implementation**

Combinational Logic Implementation

- Multiplexer Approach 1

- Implement m functions of n variables with:
 - Sum-of-minterms expressions
 - An m -wide 2^n -to-1-line multiplexer
- Design:
 - Find the truth table for the functions.
 - In the order they appear in the truth table:
 - Apply the function input variables to the multiplexer inputs S_{n-1}, \dots, S_0
 - Label the outputs of the multiplexer with the output variables
 - Value-fix the information inputs to the multiplexer using the values from the truth table (for don't cares, apply either 0 or 1)

Examples of Multiplexers – 2-1

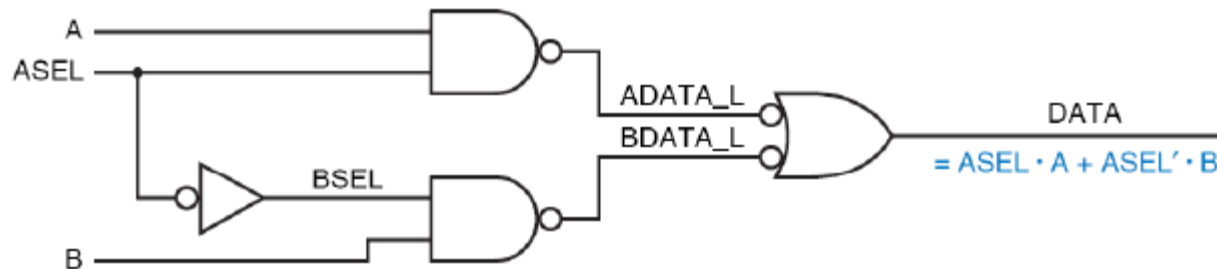 


Encoder vs Decoder

Encoders vs. Decoders




Decoders

 - N inputs, 2^N outputs
- One-hot outputs: only one output HIGH at once




A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

Decoder Implementation

 


Logic Using Decoders

- OR minterms

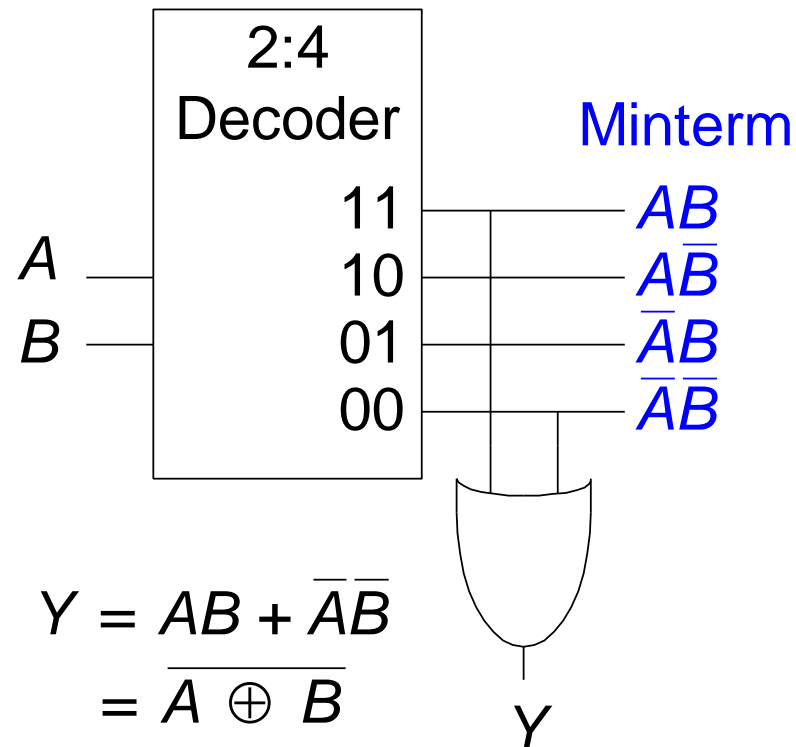

Decoder Example

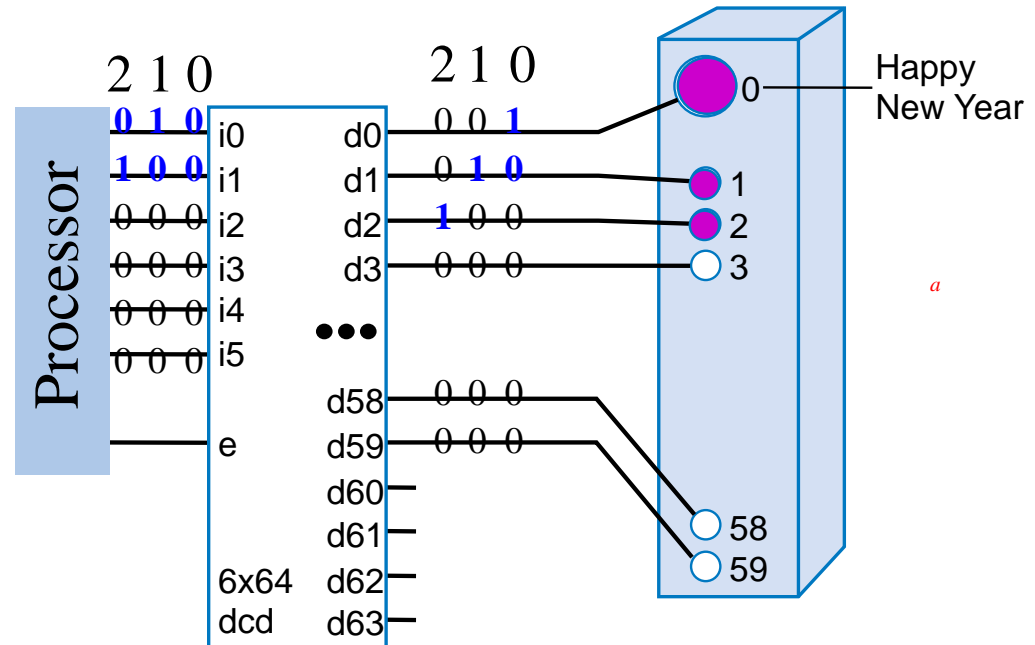- New Year's Eve Countdown Display
 - Microprocessor counts from 59 down to 0 in binary on 6-bit output
 - Want illuminate one of 60 lights for each binary number
 - Use 6x64 decoder
 - 4 outputs unused




Decoder Applications


- Selecting different banks of memory
- Selecting different devices
- Instruction decoding

BCD To 7 segment

 - BCD are 4 bit
- Design a decoder to drive 7 segment LED



Seven Segment Display

 


Activation of LEDs

- 0 : a,b,c,d,e,f
- 1: b,c
- 2:a,b,g,e,d
- 3:a,b,g,c,d
- 4:f,g,b,c
- 5:a,f,g,c,d
- 6:a,f,g,c,d,e
- 7:a,b,c
- 8:a,b,c,d,e,f,g
- 9:a,b,c,d,f,g

Decoder Expansion - Example 1

■ Result

 


Decoder Expansion - Example 2

- **7-to-128-line decoder**
 - Number of output ANDs = 128
 - Number of inputs to decoders driving output ANDs = 7
 - Closest possible split to equal
 - 4-to-16-line decoder
 - 3-to-8-line decoder
 - 4-to-16-line decoder
 - Number of output ANDs = 16
 - Number of inputs to decoders driving output ANDs = 2
 - Closest possible split to equal
 - 2 2-to-4-line decoders
 - Complete using known 3-8 and 2-to-4 line decoders

Encoding

- **Encoding - the opposite of decoding - the conversion of an m -bit input code to a n -bit output code with $n \leq m \leq 2^n$ such that each valid code word produces a unique output code**
- **Circuits that perform encoding are called *encoders***
- **An encoder has 2^n (or fewer) input lines and n output lines which generate the binary code corresponding to the input values**
- **Typically, an encoder converts a code containing exactly one bit that is 1 to a binary code corresponding to the position in which the 1 appears.**


Binary Encoder

 

Binary Encoder

8-to-3 binary encoders

I0	I1	I2	I3	I4	I5	I6	I7	Y2	Y1	Y0
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

 

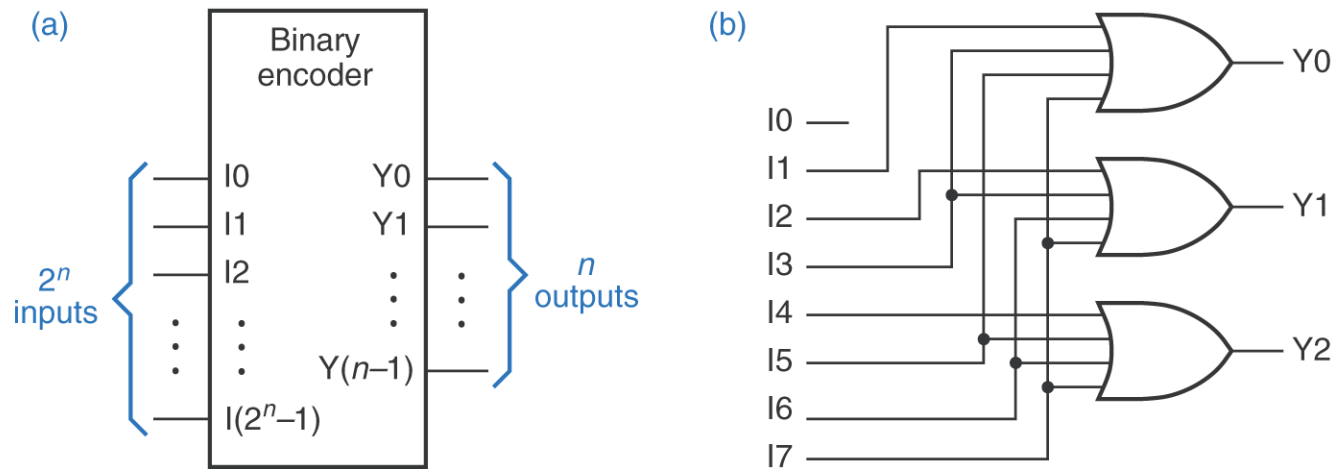


Figure 6-45

Binary encoder: (a) general structure; (b) 8-to-3 encoder.

 


Figure 6-46

A system with 2^n requestors, and a “request encoder” that indicates which request signal is asserted at any time.

Encoder Example

- **A decimal-to-BCD encoder**
 - **Inputs:** 10 bits corresponding to decimal digits 0 through 9, (D_0, \dots, D_9)
 - **Outputs:** 4 bits with BCD codes
 - **Function:** If input bit D_i is a 1, then the output (A_3, A_2, A_1, A_0) is the BCD code for i ,
- **The truth table could be formed, but alternatively, the equations for each of the four outputs can be obtained directly.**

Encoder Example (continued)

- Input D_i is a term in equation A_j if bit A_j is 1 in the binary value for i .
- Equations:
$$A_3 = D_8 + D_9$$
$$A_2 = D_4 + D_5 + D_6 + D_7$$
$$A_1 = D_2 + D_3 + D_6 + D_7$$
$$A_0 = D_1 + D_3 + D_5 + D_7 + D_9$$
- $F_1 = D_6 + D_7$ can be extracted from A_2 and A_1

Priority Encoder

- If more than one input value is 1, then the encoder just designed does not work.
- One encoder that can accept all possible combinations of input values and produce a meaningful result is a *priority encoder*.
- Among the 1s that appear, it selects the most significant input position (or the least significant input position) containing a 1 and responds with the corresponding binary code for that position.

Priority Encoder (Mano)

□ **TABLE 3-8**
Truth Table of Priority Encoder

Inputs				Outputs		
D_3	D_2	D_1	D_0	A_1	A_0	V
0	0	0	0	X	X	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1

Priority Encoder Example

- Priority encoder with 5 inputs (D_4, D_3, D_2, D_1, D_0) - highest priority to most significant 1 present - Code outputs A_2, A_1, A_0 and V where V indicates at least one 1 present.

No. of Min-terms/Row	Inputs					Outputs			
	D_4	D_3	D_2	D_1	D_0	A_2	A_1	A_0	V
1	0	0	0	0	0	X	X	X	0
1	0	0	0	0	1	0	0	0	1
2	0	0	0	1	X	0	0	1	1
4	0	0	1	X	X	0	1	0	1
8	0	1	X	X	X	0	1	1	1
16	1	X	X	X	X	1	0	0	1

- Xs in input part of table represent 0 or 1; thus table entries correspond to product terms instead of minterms.

Priority Encoder Example (continued)

- Could use a K-map to get equations, but can be read directly from table and manually optimized if careful:


$$A_2 = D_4$$

$$A_1 = \overline{D}_4 D_3 + \overline{D}_4 \overline{D}_3 D_2 = \overline{D}_4 F_1, \quad F_1 = (D_3 + D_2)$$

$$A_0 = \overline{D}_4 D_3 + \overline{D}_4 \overline{D}_3 \overline{D}_2 D_1 = \overline{D}_4 (D_3 + \overline{D}_2 D_1)$$


$$V = D_4 + F_1 + D_1 + D_0$$

Priority Encoder (Mano)

 


Timing

 - Delay between input change and output changing
- How to build fast circuits?




Output Timing Constraints

 - **Propagation delay:** t_{pcq} = time after clock edge that the output Q is guaranteed to be stable (i.e., to stop changing)
- **Contamination delay:** t_{ccq} = time after clock edge that Q might be unstable (i.e., start changing)



Propagation & Contamination Delay

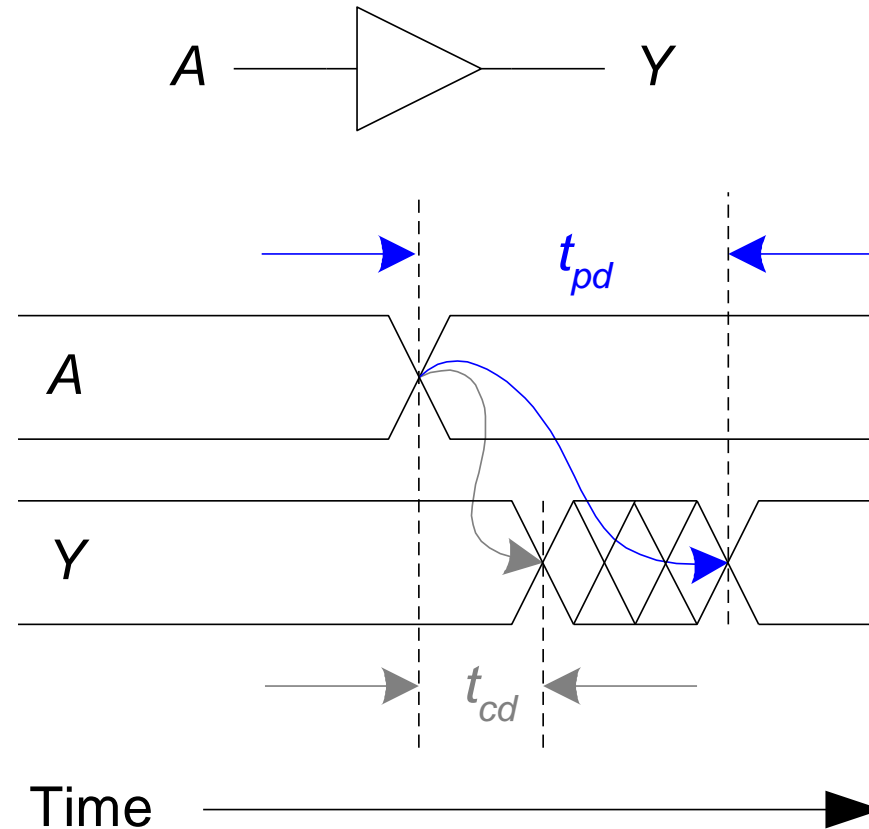- **Propagation delay:** t_{pd} = max delay from input to output
- **Contamination delay:** t_{cd} = min delay from input to output




Propagation & Contamination Delay

- Delay is caused by
 - Capacitance and resistance in a circuit
 - Speed of light limitation
- Reasons why t_{pd} and t_{cd} may be different:
 - Different rising and falling delays
 - Multiple inputs and outputs, some of which are faster than others
 - Circuits slow down when hot and speed up when cold



Critical (Long) & Short Paths

 

Critical (Long) Path: $t_{pd} = 2t_{pd_AND} + t_{pd_OR}$


Short Path: $t_{cd} = t_{cd_AND}$

Glitches

- When a single input change causes an output to change multiple times

Glitch Example


 
- What happens when $A = 0$, $C = 1$, B falls?





		AB			
		00	01	11	10
C	0	1	0	0	0
	1	1	1	1	0

$$Y = \bar{A}\bar{B} + BC$$

Glitch Example (cont.)

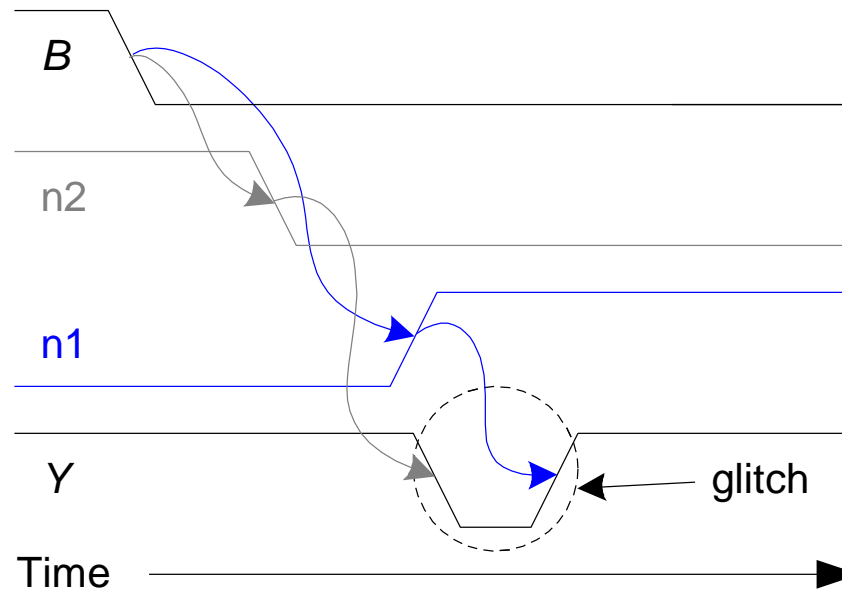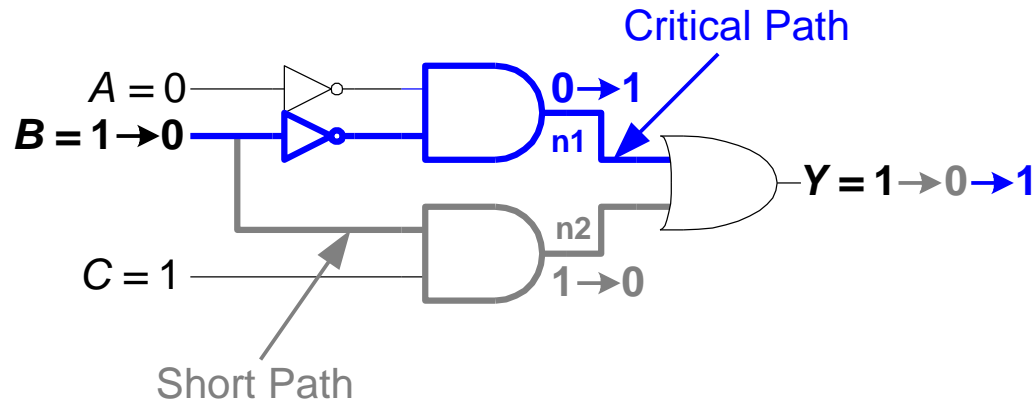

Fixing the Glitch

 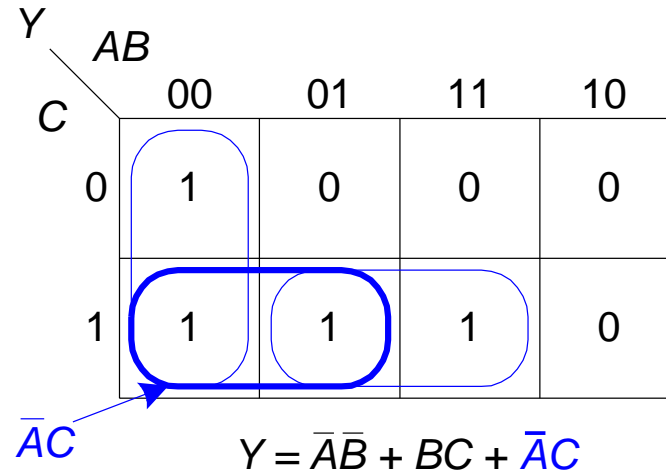

Why Understand Glitches?

- Glitches don't cause problems because of **synchronous design** conventions (see Chapter 3)
- It's important to **recognize** a glitch: in simulations or on oscilloscope
- Can't get rid of all glitches – simultaneous transitions on multiple inputs can also cause glitches



Timing Hazard

- We have studied **steady-state** behavior
 - Assuming inputs have been stable for a long time
- The **transient behavior** of circuits may differ
 - A circuit's output may produce a pulse, called a **glitch**
- A **hazard** is said to exist when a circuit has a possibility of producing a glitch


Static and Dynamic Hazard

- **Static-1**: circuit may produce a 0 glitch when we expect a steady 1 at the output
 - A pair of inputs combinations
 - both give a 1 output
 - differ in only one input variable
 - May produce a momentary 0 output when the transition takes place
- **Static-0**: circuit may produce a 1 glitch when we expect a steady 0 at the output
 - Properly designed AND-OR circuits do not have static-0 hazards
- A **dynamic hazard** is the possibility of an output changing **more than once** as the result of a single input transition

Static-1 Hazard

- Input combination differ in only one input variable
- Both give 1 output and there's a possibility of momentary 0
- AND-OR
- $X,Y,Z = 111$ and $X,Y,Z=110$

(a)

 

(b)

 


Figure 4-38

Circuit with a static-1 hazard: (a) logic diagram; (b) timing diagram.

Static-0 Hazard

- Input combination differ in only one input variable
- Both give 0 output and there's a possibility of momentary 1
- OR-AND combination
- $W, X, Y = 000$ and Z is changed



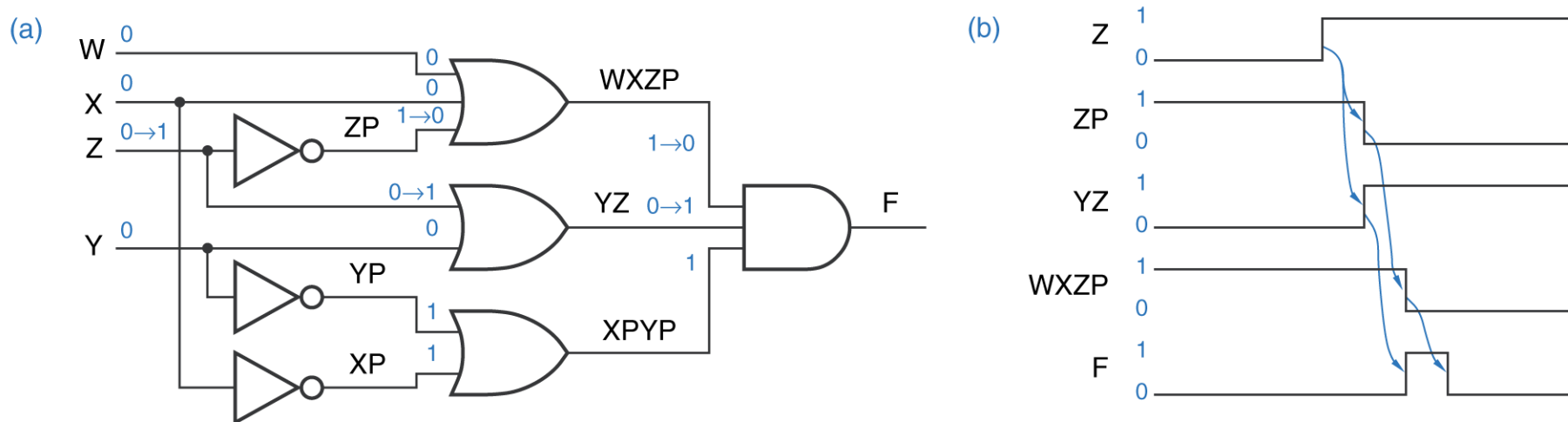


Figure 4-39

 Circuit with static-0 hazards: (a) logic diagram; (b) timing diagram.



$$F = X \cdot Z' + Y \cdot Z$$

 

$$F = X \cdot Z' + Y \cdot Z + X \cdot Y$$

Figure 4-40

Karnaugh map for the circuit of Figure 4-38: (a) as originally designed;
 (b) with static-1 hazard eliminated.

Static-1 Hazard

- Properly designed AND-OR has no Static-0 Hazard but may have Static-1 Hazard
- $X,Y,Z=111, X,Y,Z=110$
- Output could glitch to 0 before the other input combination goes to 1
- Add an extra term – consensus term



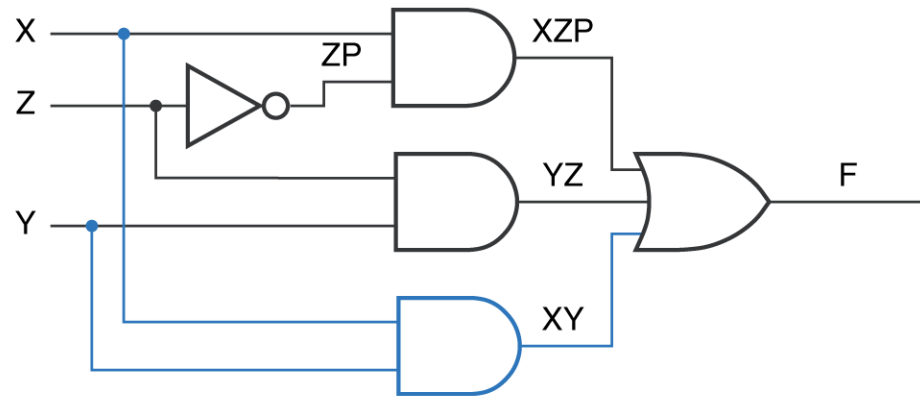


Figure 4-41
Circuit with static-1 hazard eliminated.

 
 
$$F = X \cdot Y' \cdot Z' + W' \cdot Z + W \cdot Y$$



$$F = X \cdot Y' \cdot Z' + W' \cdot Z + W \cdot Y + W' \cdot X \cdot Y' + Y \cdot Z + W \cdot X \cdot Z'$$

Figure 4-42

Karnaugh map for another sum-of-products circuit:(a) as originally designed;
(b) with extra product terms to cover static-1 hazards.

Dynamic Hazard

- Dynamic Hazards do not occur in a properly designed two level AND-OR or OR-AND circuits
- Finding Hazards are hard
- Hazard analysis is needed only in asynchronous sequential circuits and not needed in synchronous circuits as the outputs are not looked at until the clock edge

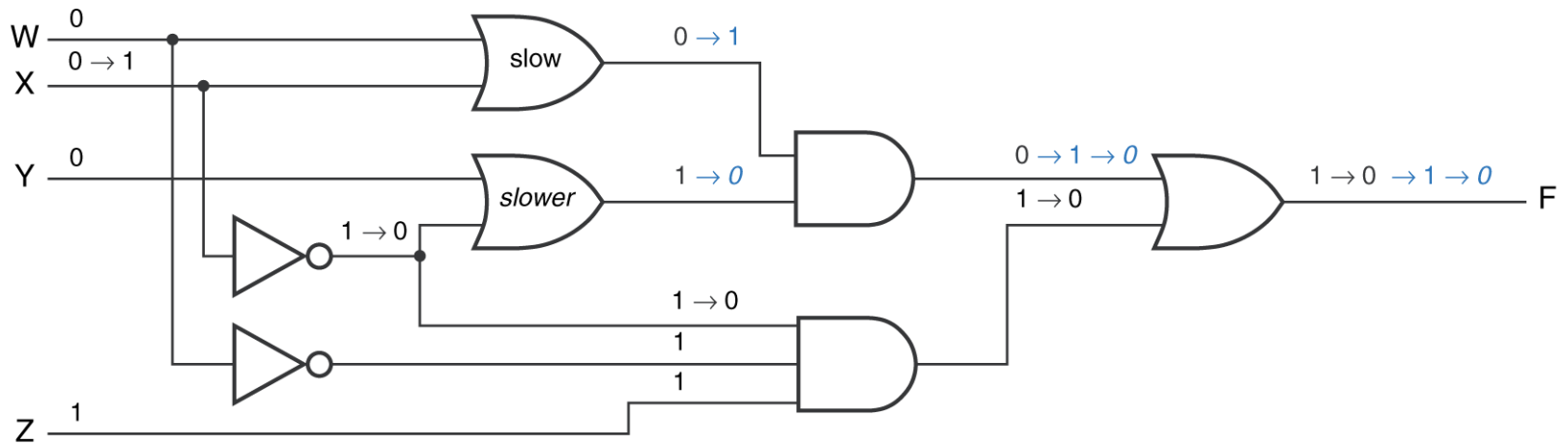


Figure 4-43
Circuit with a dynamic hazard.