
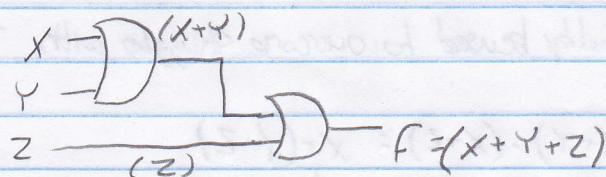



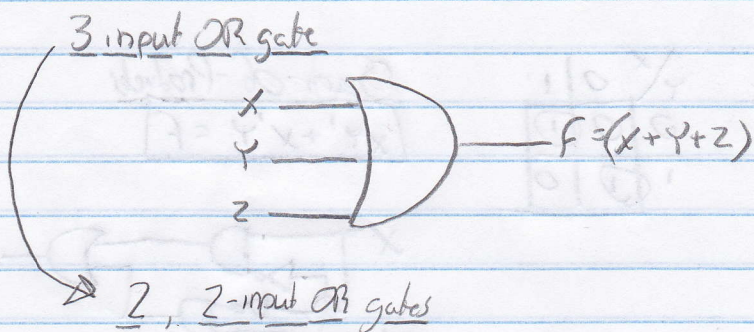
[4.25] n -input OR gate $\Rightarrow (n-1)$ 2-input OR gates



* An n -input NOR gate cannot be transformed using the same expression

3-input NOR Gate

2, 2-input NOR Gates

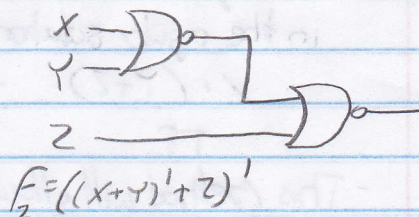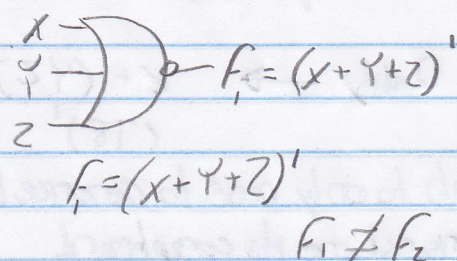

[4.30] Use switching algebra to rewrite the following using as few inversions as possible (complemented parentheses are OK)...

$$B' \cdot C + A \cdot C \cdot D' + A' \cdot C + E \cdot B' + E \cdot (A + C) \cdot (A' + D')$$

$$E(B' + (A + C)(A' + D')) + C(B' + AD' + A')$$

$$E(B' + \cancel{A} + AD' + CA' + CD') + CB' + CAD' + CA'$$

$$EB' + [EAD' + \cancel{E}A' + ECD'] + CB' + CAD' + \cancel{CA'}$$

$$A'(EC + C) = A'C \rightarrow A'C + EB' + EAD' + ECD' + CB' + CAD'$$

$$D'(EA + EC) = A'C + EB' + CB' + CAD'$$

$$[D'(EA + EC) + B'(E + C) + A'C + CAD'] = 4 \text{ Inversions}$$

[4.35] Exclusive OR = XOR, 2-input gate. Output is one if only one of its inputs is 1. Write truth table, sum-of-products, and corresponding AND-OR circuit for XOR function


Truth Table

X	Y	XOR
0	0	0
0	1	1
1	0	1
1	1	0

X	Y	XOR
0	0	0
0	1	1
1	0	1
1	1	0

Sum-of-Products

$$XY' + X'Y = F$$

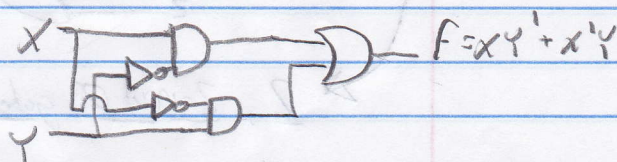

[4.46] How can duality be used to overcome struggles with Theorem T8'?

$$(T8') = (X+Y) \cdot (X+Z) = X + (Y \cdot Z)$$

- Because students have no problem utilizing the regular Theorem T8 and its outcome $(X \cdot (Y+Z))$, they can use duality to basically derive the solution to $T8'$ by flipping the And's and OR's in the regular solution.

$$X \cdot (Y+Z) \xrightarrow{\text{Duality}} X + (Y \cdot Z)$$

$T8 \qquad \qquad \qquad (T8)'$

- This method will allow students to only need to remember the original T8 instead of both the original and its complement.

[4.54] $F = \sum wxyz(2,3,8,9)$


$$F = w'x'y + wx'y'$$

$$x'(w'y + wy')$$


wz	00	01	11	10
00	0	0	0	1
01	0	0	0	1
11	1	0	0	0
10	1	0	0	0

Next
Page

Page Two

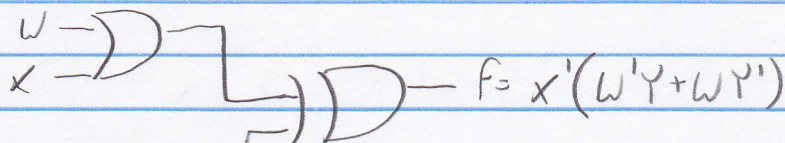

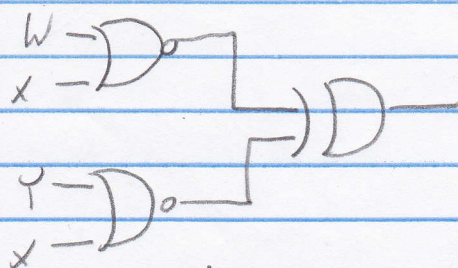* - What is the solution if the OR gates are changed to NOR gates?



X	Y	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

W	X	Y	WXNOR	YNOR	XOR
0	0	0	1	1	0
0	0	1	1	0	1
0	1	0	0	0	0
0	1	1	0	0	0
1	0	0	0	1	1
1	0	1	0	0	0
1	1	0	0	0	0
1	1	1	0	0	0

$$= WX'Y(WX'YZ \& WX'YZ')$$

$$= WX'Y'(WX'YZ \& WX'YZ')$$

The solution is the same

[4.57] Prove whether the following is a minimal sum algebraically
 $F = (S'TUVW) + (S'TU'WY) + (S'TUVX'Y)$

$$F = (S'TW)(UV + U'Y + VX'Y)$$

$$F = (S'TW)(UV + U'Y + (U + U')(UX'Y))$$

$$= (S'TW)(UV + U'Y + UVX'Y + U'UX'Y)$$

$$= (S'TW)(UV(1 + X'Y) + U'Y(1 + VX'))$$

$$= (S'TW)(UV + U'Y) = \text{minimal sum}$$