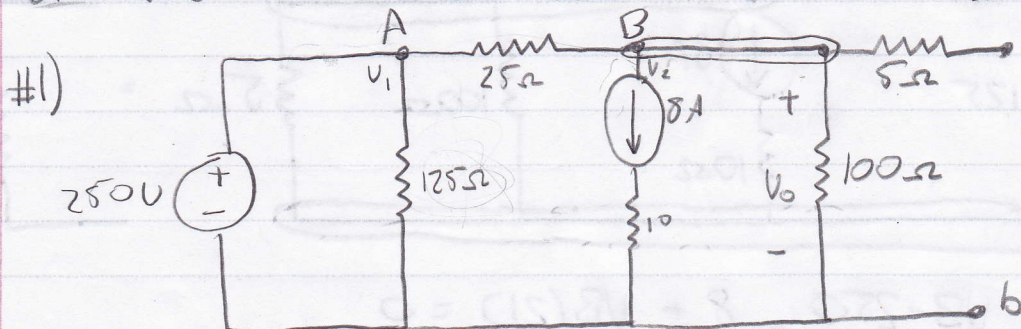


Brain faure 150003563 PEE HW#6 Due 10/27/2014




a)  $V_A = 250$   $\frac{V_B - 250}{25} + 8 + \frac{V_B}{100} = 0$

$\frac{4V_B}{100} + \frac{V_B}{100} - 10 + 8 = 0$   $\frac{5V_B}{100} = 2$   $V_B = \frac{200}{5}$   $V_B = 40$


$V_0 = V_B - 0 = V_B$  \* \*

$V_0 = 40 \text{ volts}$  (short circuit current is written after part B, sorry I missed the question) \* \*

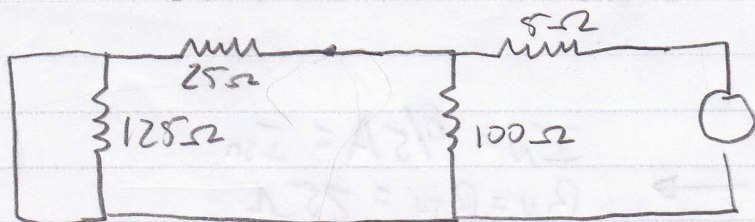
b) You turn all voltage sources into shorts & all current sources into open circuits to find the thevenin resistance...



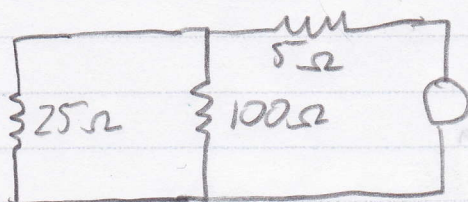- Next step is to retrace the 125Ω resistor because all current will travel through the short



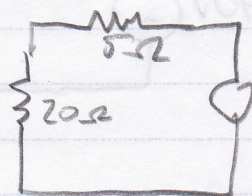$\left( \frac{4}{100} + \frac{1}{100} \right) = 20\Omega$




$20 + 5 = 25\Omega = R_{eq}$

\* a. cont.) Short circuit current, short the a & b nodes and solve for current through wire





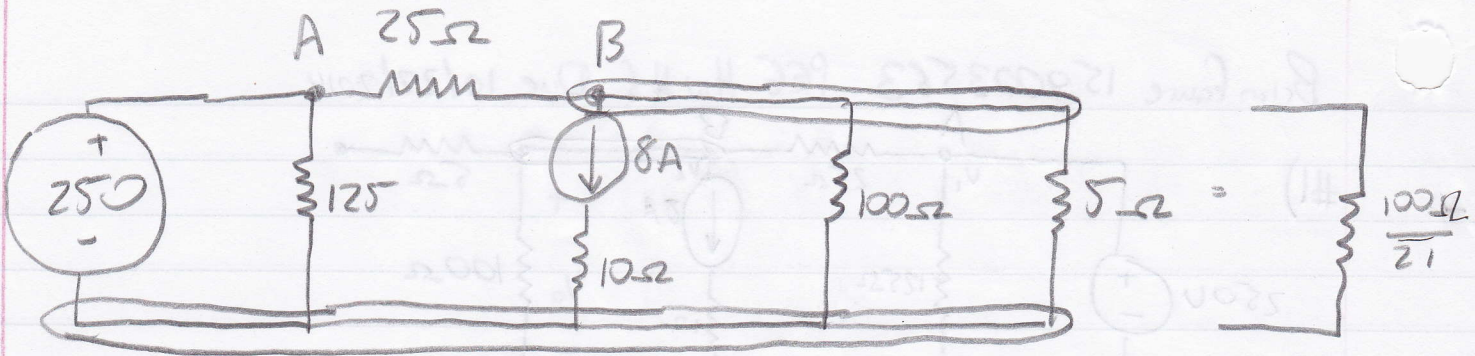
$$100\Omega // 5\Omega = \left(\frac{1}{100} + \frac{20}{100}\right)^{-1} = \frac{100}{21}\Omega$$



$$V_A = 250V$$


$$\frac{V_B - 250}{25} + 8 + \frac{V_B}{100} = 0$$
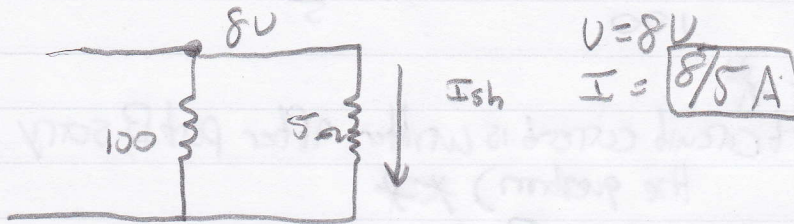
$$\frac{25V_B}{100} = 2 \quad 25V_B = 200 \quad V_B = 8$$



C.) Draw the norton equivalent of the circuit


Thevenin

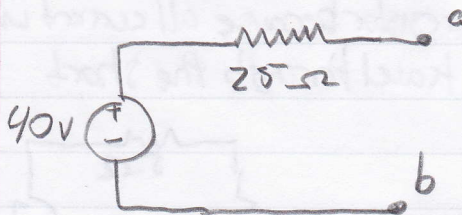

$$I_N = 8/5A = I_{sh}$$

$$R_N = R_{TH} = 25\Omega$$

Norton

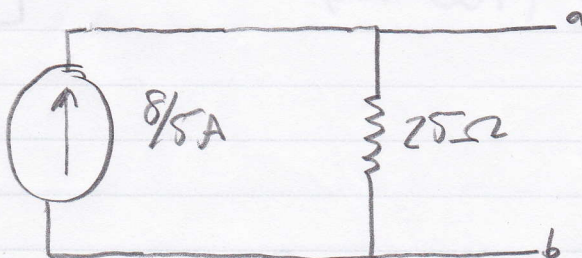




Pg 2

d.) If load  $60\Omega$  connected to norton eq. what is the power delivered to the load? Explain

$$P = V^2/R = I^2 R$$

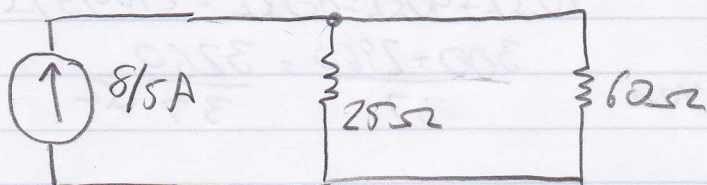

Current divider  

$$\left(\frac{25}{85}\right) \left(\frac{8}{5}\right) = I$$

$$I = \frac{40}{85} A = \frac{8}{17} A \quad P = (I^2)(R) = \left(\frac{64}{289}\right)(60) = \frac{3840}{60}$$

$$P = \frac{3840}{289} \text{ Watts}$$

(Took current divider then used  $I^2 R$  to achieve answer)

e.) The power consumed by the  $25\Omega$  resistor would be...




Current Divider

$$\left(\frac{60}{85}\right) \left(\frac{8}{5}\right) = I \quad I = \frac{96}{85} A \quad P = \left(\frac{9216}{7225}\right)(25)$$

$$P = \frac{230400}{7225} \text{ Watts} \approx 31.889$$

#2) Use superposition to find the current through  $20\Omega$  resistor...

Case One (only 40V source)

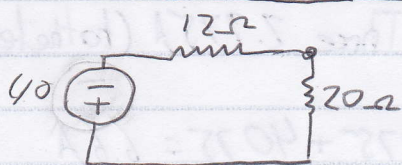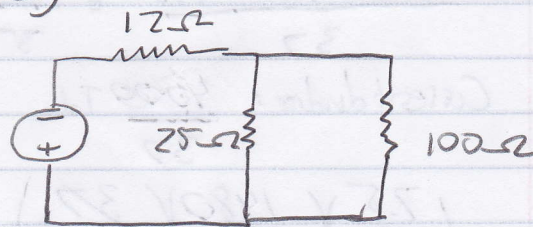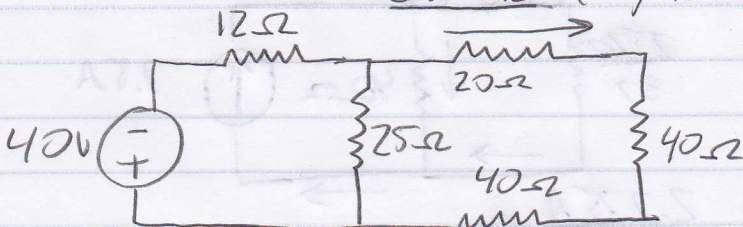

$$R_{eq} = 32\Omega$$

$$I_{in} = 40/32 A = 5/4 A$$

Current Divider  $\rightarrow \left(\frac{5}{4}\right) \left(\frac{25}{125}\right) = 1/4 A$


$$\left(\frac{1}{25} + \frac{1}{100}\right)^{-1} = 20\Omega$$

[Case one:  $1/4 A$   
(left to right)]



Case one:  $\frac{1}{4}A \rightarrow$


Case Two (only 5A source)

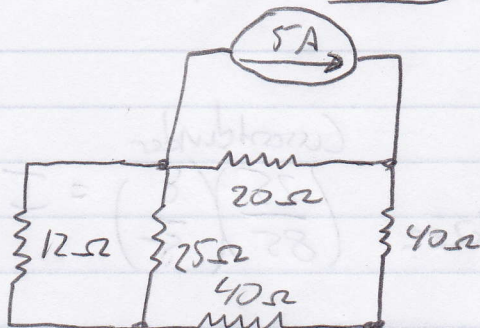

$$\left(\frac{1}{12} + \frac{1}{25}\right)^{-1} = 300/37 \Omega$$

$$40\Omega + 40\Omega = 80\Omega = 2960/37\Omega$$
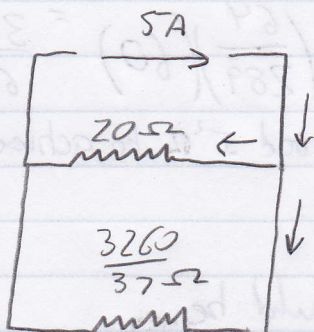
$$\frac{300 + 2960}{37} = \frac{3260}{37} \Omega$$





Current divider:  $20 = \frac{740}{37} \parallel \frac{740 + 3260}{37}$

$$= \frac{4000}{37} \rightarrow \left(\frac{5A}{1}\right) \left(\frac{3260}{37} \cdot \frac{37}{4000}\right)$$

$$= \frac{5}{1} \cdot \frac{3260}{4000} = 4.075A$$

[Case Two: 4.075A (to the left)] ←


Case Three (only 7.5A source)

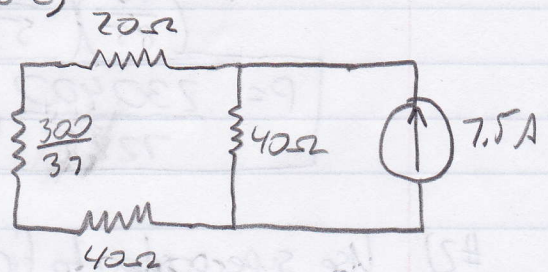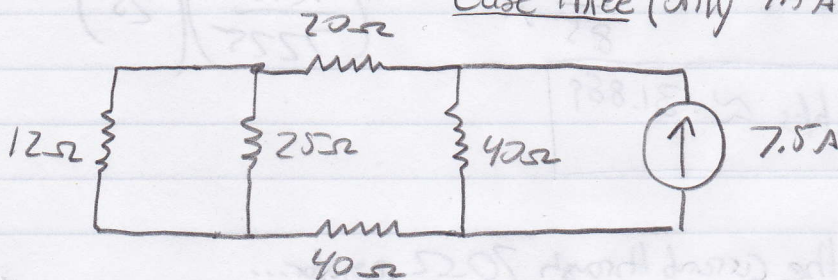

$$\frac{300 + 740 + 1480}{37} = \frac{2520}{37}$$

Current divider:  $\frac{4000}{37} \text{ Tot}$
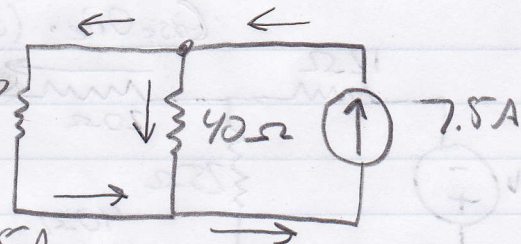
$$\left(\frac{7.5}{1}\right) \left(\frac{1480}{37} \cdot \frac{37}{4000}\right) = 2.775A$$



[Case Three 2.775A (to the left)]


-Tot. Current in 20Ω resistor =  $-0.25 + 2.775 + 4.075 = 6.6A$

6.6A




Pg 3
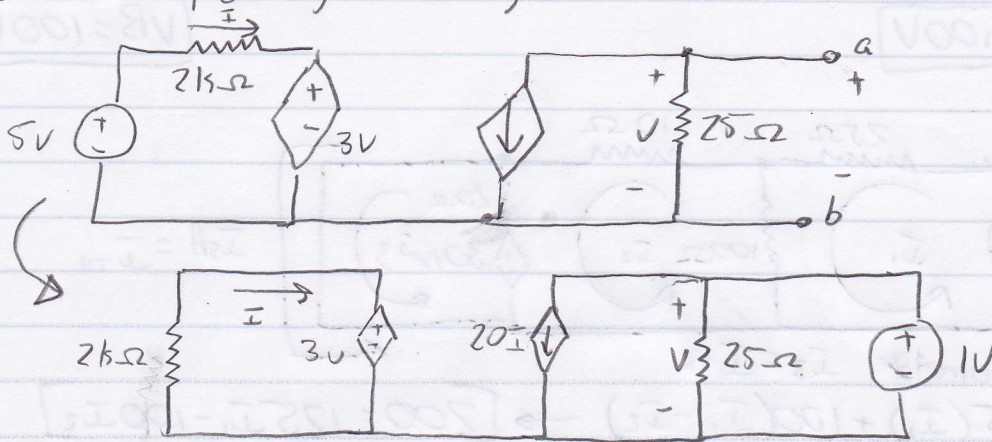
#3) Find  $R_{eq}$  directly for following circuit



$$V = 1 \text{ Volt}$$

$$I = \frac{-3}{2000}$$

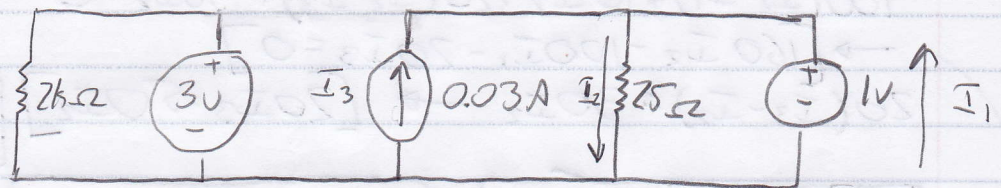


$$I_2 = \frac{1}{25} = 0.04$$

$$I_3 = 0.03A$$

$$I_1 = I_2 - I_3 = 0.04 - 0.03 = 0.01A = I$$

$$R_{TH} = \frac{1V}{0.01A} = 100\Omega = R_{TH} = R_{eq}$$
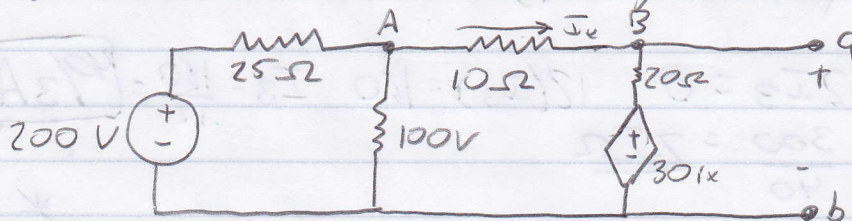
#4) Need to model the power consumed by resistor load as a function



Finding  $V_{TH}$ :  $V_B = V_{oc} = V_{TH}$

$$\frac{V_A - 200}{25} + \frac{V_A}{100} + \frac{V_A - V_B}{10} = 0 \quad \left[ \frac{15V_A}{100} = 8 + \frac{V_B}{10} \right]$$

$$\frac{V_B - V_A}{10} + \frac{V_B - 30ix}{20} = 0 \quad I_x = \frac{V_A - V_B}{10} \quad \left[ \frac{3V_B}{20} - \frac{V_A}{10} - \frac{30V_A}{200} + \frac{30V_B}{200} = 0 \right]$$

$$\frac{60V_B}{200} = \frac{50V_A}{200} \quad 60V_B = 50V_A$$

$$V_A = \frac{60V_B}{50}$$


$$V_B = \frac{50V_A}{60}$$



- Plugging that into initial eq...  $\frac{90VA - 80VA}{600} = 8 \quad \frac{40VA}{600} = 8 \quad \boxed{VA = 120V}$

$\boxed{V_{TH} = V_B = 100V}$

$\boxed{V_B = 100V}$

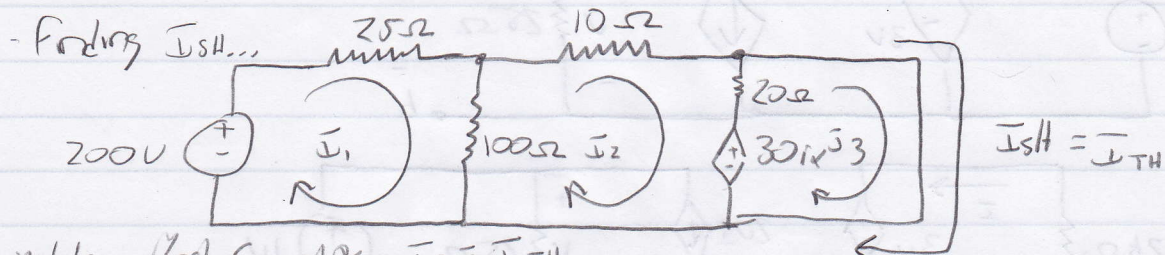

\* Using Mesh Currents  $I_3 = I_{TH}$

$200 = 25(I_1) + 100(I_1 - I_2) \rightarrow \boxed{200 = 125I_1 - 100I_2}$

$100(I_2 - I_1) + 10I_2 + 20(I_2 - I_3) + 30I_2 = 0$

$\rightarrow \boxed{160I_2 - 100I_1 - 20I_3 = 0}$

$20(I_3 - I_2) = 30I_2 \rightarrow \boxed{20I_3 = 50I_2} \quad \boxed{I_3 = \frac{50I_2}{20}} \quad \boxed{I_2 = \frac{20I_3}{50}}$

$\boxed{I_1 = \frac{200 + 100I_2}{125}}$

$\boxed{I_2 = \frac{125I_1 - 200}{100}}$

$I_1 = \frac{200}{125} + \frac{100(20I_3)}{50(125)} = \boxed{I_1 = 1.6 + 0.32I_3}$


$(160)(20I_3) - 100(1.6 + 0.32I_3) - 20I_3 = 0$

$50$

$44I_3 - 160 - 32I_3 = 0 \quad 12(I_3) = 160 \quad I_3 = \frac{160}{12} = \boxed{\frac{40}{3}A = I_3}$

$R_{TH} = \frac{100}{1} \cdot \frac{3}{40} = \frac{300}{40} = \boxed{7.5\Omega}$

Final Circuit

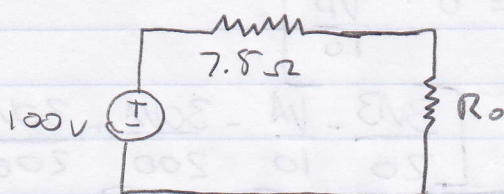

$I = \frac{100}{7.5 + R_o} \quad P = I^2 R$

$\boxed{P(R_o) = \left(\frac{100}{7.5 + R_o}\right)^2 (R_o)}$